

Mid Semester Examination Sept. 2025

Name of the Program: **B-TECH (CSE)**

Semester: **3rd**

Name of the Course: **Logic Design and Computer Organization**

Course Code: **TCS 308**

Time: 90 Minutes

Maximum Marks: 50

Note:

- (i) Answer all the questions by choosing any one of the sub questions.
- (ii) Each question carries 10 marks

Q1	(10 marks)	
(a)	Simplify the following expression using K-Map method $F(A,B,C,D, E) = \prod M(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$	
OR		CO1
(b)	Implement BCD adder and explain with the help of suitable examples.	
Q2	(10 marks)	
(a)	What are the limitations of normal encoder? Implement priority encoder.	
OR		CO1
(b)	Implement 3:8 decoder using 1:2 decoder only.	
Q3	(10 marks)	
(a)	Design a 3 bit code converter which converts binary code to gray code using suitable D-MUX.	CO1
OR		
(b)	Implement following expression using 4:1 MUX when (a) AB as selected lines. (b) CD as selected lines. $F(A,B,C,D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5, 8, 14)$	
Q4	(10 marks)	
(a)	Show that the characteristic equation for the complement output of a JK flip-flop is $Q'(t+1) = J'Q' + KQ$	CO2
OR		
(b)	Convert T flip flop into JK flip-flop.	
Q5	(10 marks)	
(a)	Draw and explain the circuit of 5 bit SISO right shift register.	CO3
OR		
(b)	Draw and explain the circuit of MOD 12 up asynchronous counter.	

